


國立高雄大學 101 學年度博士班招生考試試題

科目：電子學
 考試時間：100 分鐘


系所組別：電機工程學系
 本科原始成績：100 分

是否使用計算機：是


1. (15%) For the circuit shown in Fig. 1 first, evaluate $T_i(s)=V_i(s)/V_s(s)$ and the corresponding cutoff (corner) frequency. Second, evaluate $T_o(s)=V_o(s)/V_i(s)$ and the corresponding cutoff frequency. Put each of the transfer functions in the standard form and combine them to form the overall transfer function, $T(s)=T_i(s)\times T_o(s)$. Provide a Bode magnitude plot for $|T(j\omega)|$. What is the bandwidth between 3-dB cutoff points?

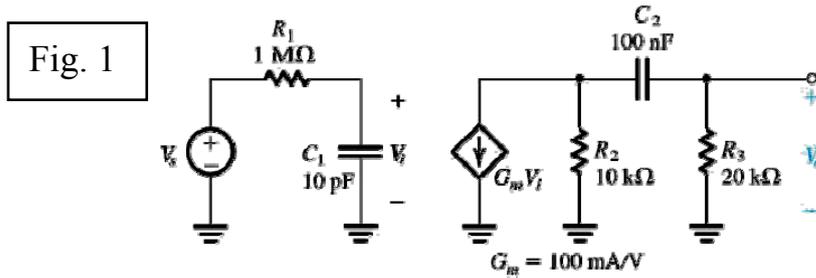

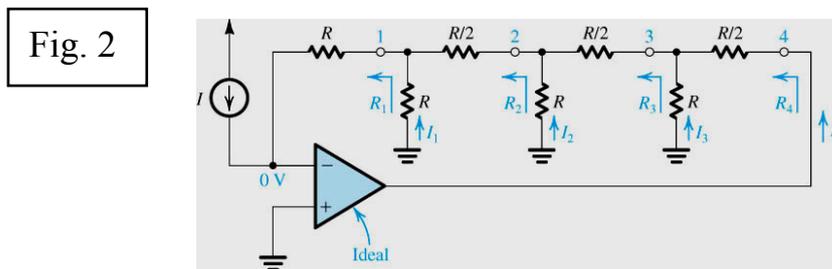2. (15%) The circuit is shown in Fig.2.
- Find the resistances looking into node 1, R_1 ; node 2, R_2 ; node 3, R_3 ; and node 4, R_4 .
 - Find the current I_1 , I_2 , I_3 , and I_4 in terms of the input current I .
 - Find the voltages at nodes 1, 2, 3, and 4, that is V_1 , V_2 , V_3 , and V_4 in terms of (IR) .



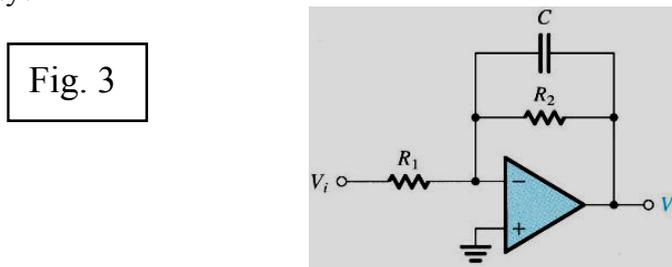3. (15%) Fig. 3 shows a circuit that performs a low-pass STC function. Such a circuit is known as a first-order low-pass active filter. Derive the transfer function, the dc gain and the 3-dB frequency. Design the circuit to obtain an input resistance of $1\text{k}\Omega$, a dc gain of 20dB, and a 3dB frequency of 4kHz. At what frequency does the magnitude of the transfer function reduce to unity?




國立高雄大學 101 學年度博士班招生考試試題

科目：電子學
 考試時間：100 分鐘


系所組別：電機工程學系
 本科原始成績：100 分

是否使用計算機：是

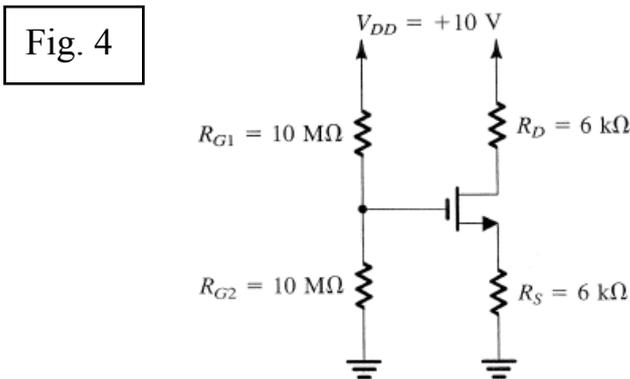4. (10%) Analyze the circuit shown in Fig. 4 to determine the voltages at all nodes and the currents through all branches. Let $V_t = 1\text{V}$ and $k'_n(W/L) = 1\text{ mA/V}^2$. Neglect the channel-length modulation effect (i.e., assume $\lambda=0$). (10%)



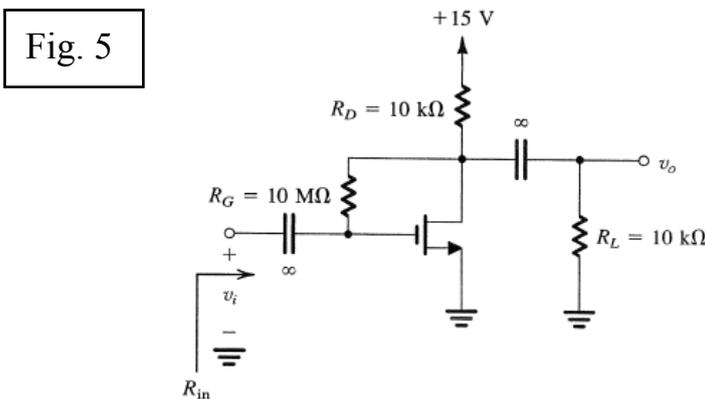5. (20%) Fig. 5 shows a discrete common-source MOSFET amplifier utilizing the drain-to-gate feedback biasing arrangement. The input signal v_i is coupled to the gate via a large capacitor, and the output signal at the drain is coupled to the load resistance R_L via another large capacitor. We wish to analyze this amplifier circuit to determine its small-signal voltage gain, its input resistance, and the largest allowable input signal. The transistor has $V_t = 1.5\text{ V}$, $k'_n(W/L) = 0.25\text{ mA/V}^2$, and $V_A = 50\text{ V}$. Assume the coupling capacitors to be sufficiently large so as to act as short circuits at the signal frequencies of interest.



國立高雄大學 101 學年度博士班招生考試試題


科目：電子學
 考試時間：100 分鐘

系所組別：電機工程學系
 本科原始成績：100 分

是否使用計算機：是

6. (15%) A MOS differential pair operated at a bias current of 0.8mA employs transistors with $W/L=100$ and $\mu_n C_{ox}=0.2\text{mA/V}^2$, using $R_D=5\text{k}\Omega$, and $R_{SS}=25\text{k}\Omega$, as shown in Fig. 6.
- Find the differential gain, the common-mode gain, and the common-mode rejection ratio (in dB) if the output is taken single-endedly and the circuit is perfectly matched.
 - Repeat (a) when the output is taken differentially.
 - Repeat (a) when the output is taken differentially but the drain resistances have a 1% mismatch.

Fig. 6

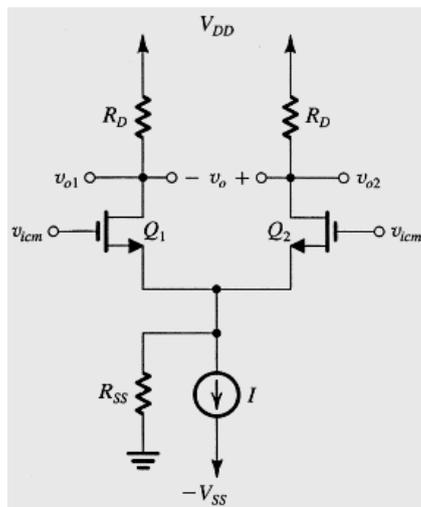

7. (10%) Sketch a CMOS logic circuit that realizes the Boolean function $Y = \overline{A + B \cdot (C+D)}$.

國立高雄大學 101 學年度博士班招生考試試題

科目：計算機概論
考試時間：100 分鐘

系所組別：電機工程學系
本科原始成績：100 分

是否使用計算機：是

1. Please explain “NP-completeness (NPC)” and give several NPC problems. (25%)
2. What is 3D IC? What are the compacts that 3D IC may bring to the IT industry? (25%)
3. What is “Quantum Computing”? What the computer organization may be in a quantum computing age? (25%)
4. Recently, major CPU manufacturers announce new APU (Accelerated Processing Unit) products to the market for the next-generation computers. Please state what an APU is and why it is the emerging trend of future computers. (25%)